

Santa Clara University  
Department of Electrical Engineering  
**ELEN 153 Digital Integrated Circuit Design**

**Pre-lab 5**  
**Input Stimulus for 4-bit Adder**

**Name:** \_\_\_\_\_

For the Lab Assignment 5, you will be entering the schematic of a 4-bit Adder. To test the correctness of the schematics entered, you need input stimulus. In the table below, work on 4-bit input vector pairs A and B to get the desired Carry and Sum outputs as described.

	<b>A</b>	<b>B</b>	<b>C<sub>4</sub>, S</b>
<b>Example</b>	0000	1010	01010
<b>1</b>			10101
<b>2</b>			01010
<b>3</b>			10101
<b>4</b>			01010
<b>5</b>			10101
<b>6</b>			01010
<b>7</b>			10101
<b>8</b>			01010
<b>9</b>			10101
<b>10</b>			01010

*Notes*

1. Maximum value of a 4-bit vector is 1111. Do not exceed the maximum by using 5-bits.
2. Each unique combination of vector pairs A and B will be worth 10 points. Simply swapping A and B values will not count as two pairs. For example, the vector pair A=0000 B=1010, and A=1010 B=0000 are not unique, so is only worth 10 points.